

Ken Sutter  
Phil Nevins  
Cody Reid  
Daniel Anishchenko


## ECE-425 Lab 1 CMOS Inverter

### 1) Cell Description: CMOS Inverter

The CMOS (Complementary Metal-Oxide-Semiconductor) inverter is a digital logic gate that performs the logical NOT operation. The CMOS inverter has one input and one output. When the input is at a low logic level, the NMOS transistor is off (open), and the PMOS transistor is on (closed). This allows current to flow from the power supply voltage (Vdd) to the output, driving it to a high logic level. The CMOS inverter is built using one NMOS and one PMOS transistor connected in series through their drains. The input of the CMOS inverter is connected to the gates of both transistors. The output of the CMOS transistor is connected to the drains of both PMOS and NMOS. The source for the NMOS is connected to ground and the source of PMOS is connected to the power supply (VDD).

### 2) Cell Symbol:

Figure 1: 50x90 CMOS Inverter TB Schematic

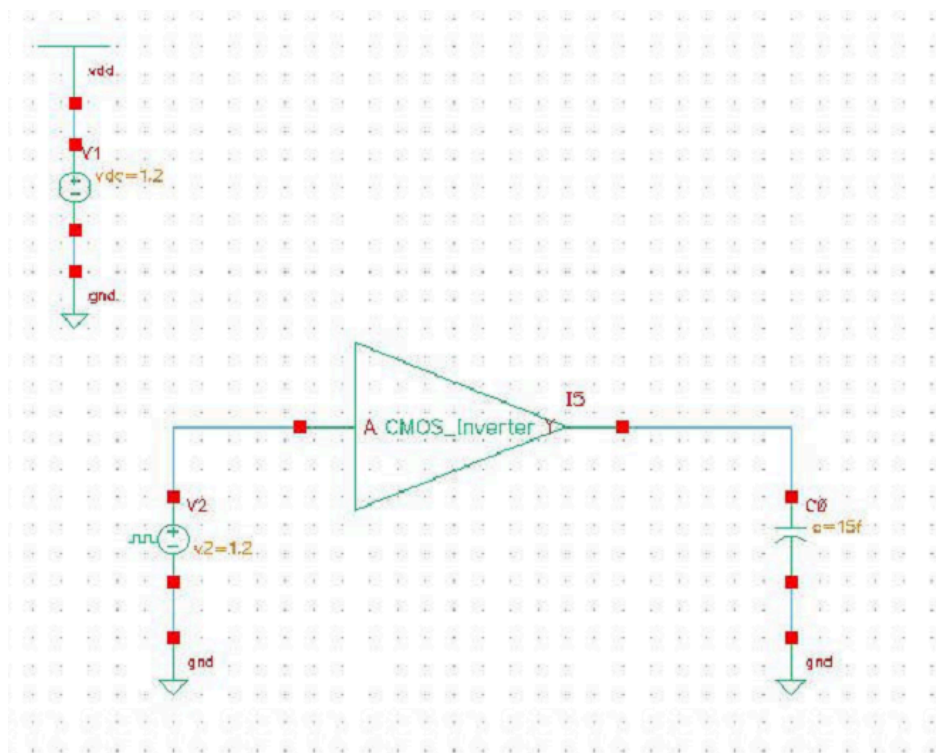


3) Cell Truth Table:

Table 1: CMOS Inverter Truth Table

| Cell Truth Table  |                    |
|-------------------|--------------------|
| Cell Inputs {0,1} | Cell Outputs {H,L} |
| 0                 | H                  |
| 1                 | L                  |

4) Cell Schematic Diagram:

Figure 2: 50x90 CMOS Inverter TB Schematic

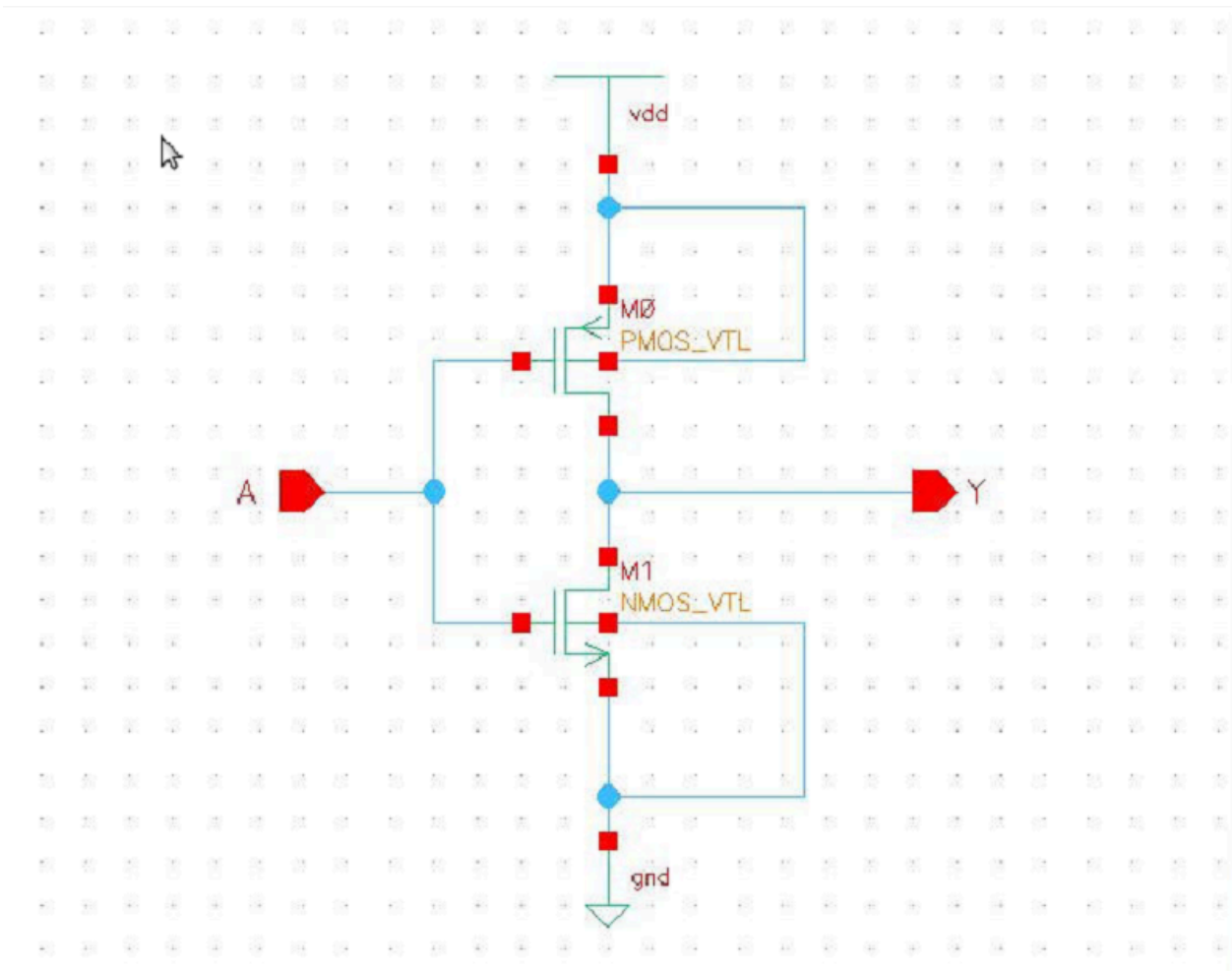

**5) Transistor Dimensions:****Table 2:** Cell and Transistor Dimensions for CMOS

| Cell Physical Dimensions        |             |            |
|---------------------------------|-------------|------------|
|                                 | X           | Y          |
| Cell Dimension in $\mu\text{m}$ | 50          | 90         |
| Transistor Dimensions           |             |            |
| Transistor Instance Number      | Length (nm) | Width (nm) |
| PMOS_VTL                        | 50          | 90         |
| NMOS_VTL                        | 50          | 90         |

**6) Input X: Output Rise Time Data  $t_r$  (ns):****Table 3:** Transistor Rise Time for CMOS Inverter

| Input X: Output Rise Time Data $t_r$ |                   |   |   |        |   |
|--------------------------------------|-------------------|---|---|--------|---|
| Input rise/fall time (ns)            | Output Load (FOx) |   |   |        |   |
|                                      | 0                 | 1 | 2 | 4      | 8 |
| 0.04                                 | -                 | - | - | 0.3949 | - |

**7) Stack S, Input X: Output Fall Time Data  $t_f$  (ns):****Table 4:** Transistor Fall Time for CMOS Inverter

| Input X: Output Fall Time Data $t_f$ |                   |   |   |        |   |
|--------------------------------------|-------------------|---|---|--------|---|
| Input rise/fall time (ns)            | Output Load (FOx) |   |   |        |   |
|                                      | 0                 | 1 | 2 | 4      | 8 |
| 0.04                                 | -                 | - | - | 0.1155 | - |

### 8) Data Worst Case Low to High Propagation Delay $t_{p_{lh}}$ (ns):

**Table 5:** Data Worst Case Low to High Propagation Delay  $t_{p_{lh}}$  (ns) for CMOS Inverter

| Data Worst Case Low to High Propagation Delay $t_{p_{lh}}$ (ns) |                   |   |   |        |   |
|---|-------------------|---|---|--------|---|
| Input rise/fall time (ns)                                       | Output Load (FOx) |   |   |        |   |
|   | 0                 | 1 | 2 | 4      | 8 |
| 0.04  | -                 | - | - | 0.0937 | - |

### 9) Data Worst Case High to Low Propagation Delay $t_{p_{hl}}$ (ns):

**Table 6:** Data Worst Case High to Low Propagation Delay  $t_{p_{hl}}$  (ns) for CMOS Inverter

| Data Worst Case Low to High Propagation Delay $t_{p_{hl}}$ (ns) |                   |   |   |       |   |
|---|-------------------|---|---|-------|---|
| Input rise/fall time (ns)                                       | Output Load (FOx) |   |   |       |   |
|   | 0                 | 1 | 2 | 4     | 8 |
| 0.04  | -                 | - | - | 0.270 | - |

### 10) Transient Analysis

**Figure 3:** 50x90 CMOS Inverter Transient Analysis - 1



 


Figure 4: 50x90 CMOS Inverter Transient Analysis - 2

 

11) DC analysis

Figure 5: 50x90 CMOS Inverter DC Analysis

 


## 1) Cell Description: CMOS Wide Inverter

The CMOS (Complementary Metal-Oxide-Semiconductor) Wide inverter is a digital logic gate that performs the logical NOT operation. The CMOS Wide inverter has one input and one output. When the input is at a low logic level, the NMOS transistor is off (open), and the PMOS transistor is on (closed). This allows current to flow from the power supply voltage (Vdd) to the output, driving it to a high logic level. The CMOS Wide inverter is built using one NMOS and one PMOS transistor connected in series through their drains. The input of the CMOS Wide inverter is connected to the gates of both transistors. The output of the CMOS Wide transistor is connected to the drains of both PMOS and NMOS. The source for the NMOS is connected to ground and the source of PMOS is connected to the power supply (VDD). The CMOS inverter is known for its low power consumption, high input impedance, and high output impedance, making it a fundamental component in modern digital integrated circuits.

## 2) Cell Symbol:

**Figure 6:** CMOS Wide Inverter Cell Symbol

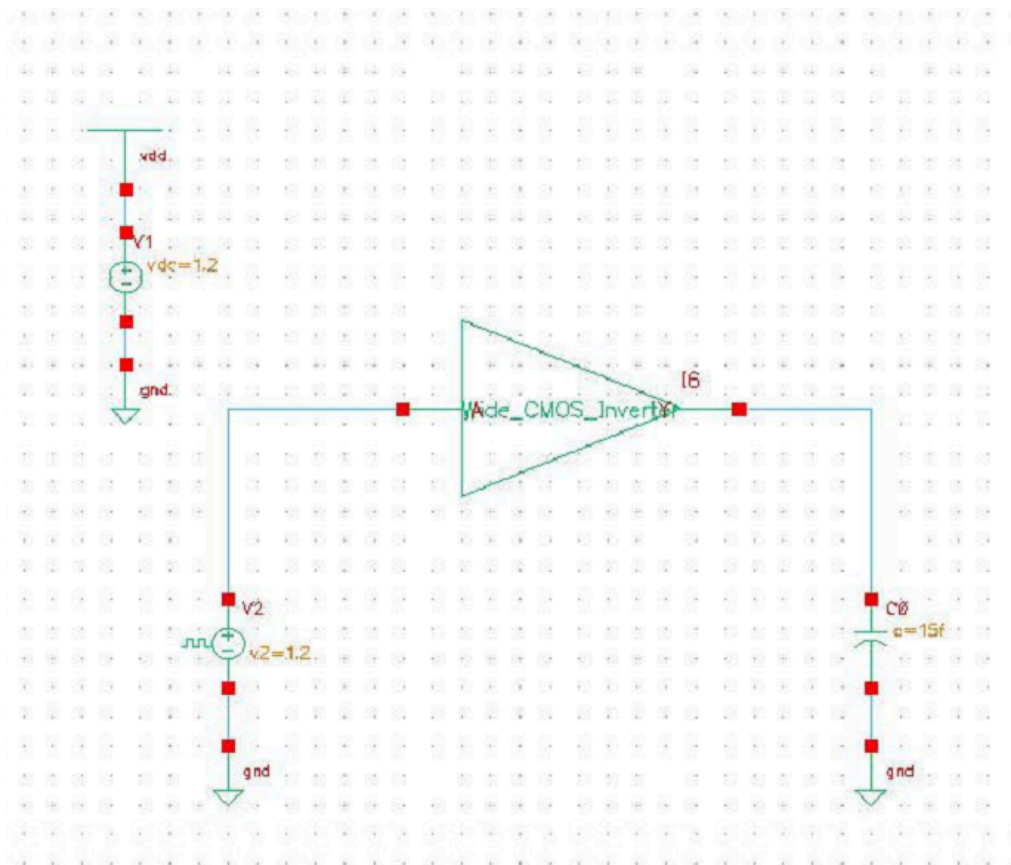


### 3) Cell Truth Table:

**Table 7: CMOS Wide Inverter Truth Table**

| Cell Truth Table  |                    |
|-------------------|--------------------|
| Cell Inputs {0,1} | Cell Outputs {H,L} |
| 0                 | H                  |
| 1                 | L                  |

### 4) Cell Schematic Diagram:

**Figure 7: 50x360 CMOS Wide Inverter Schematic**

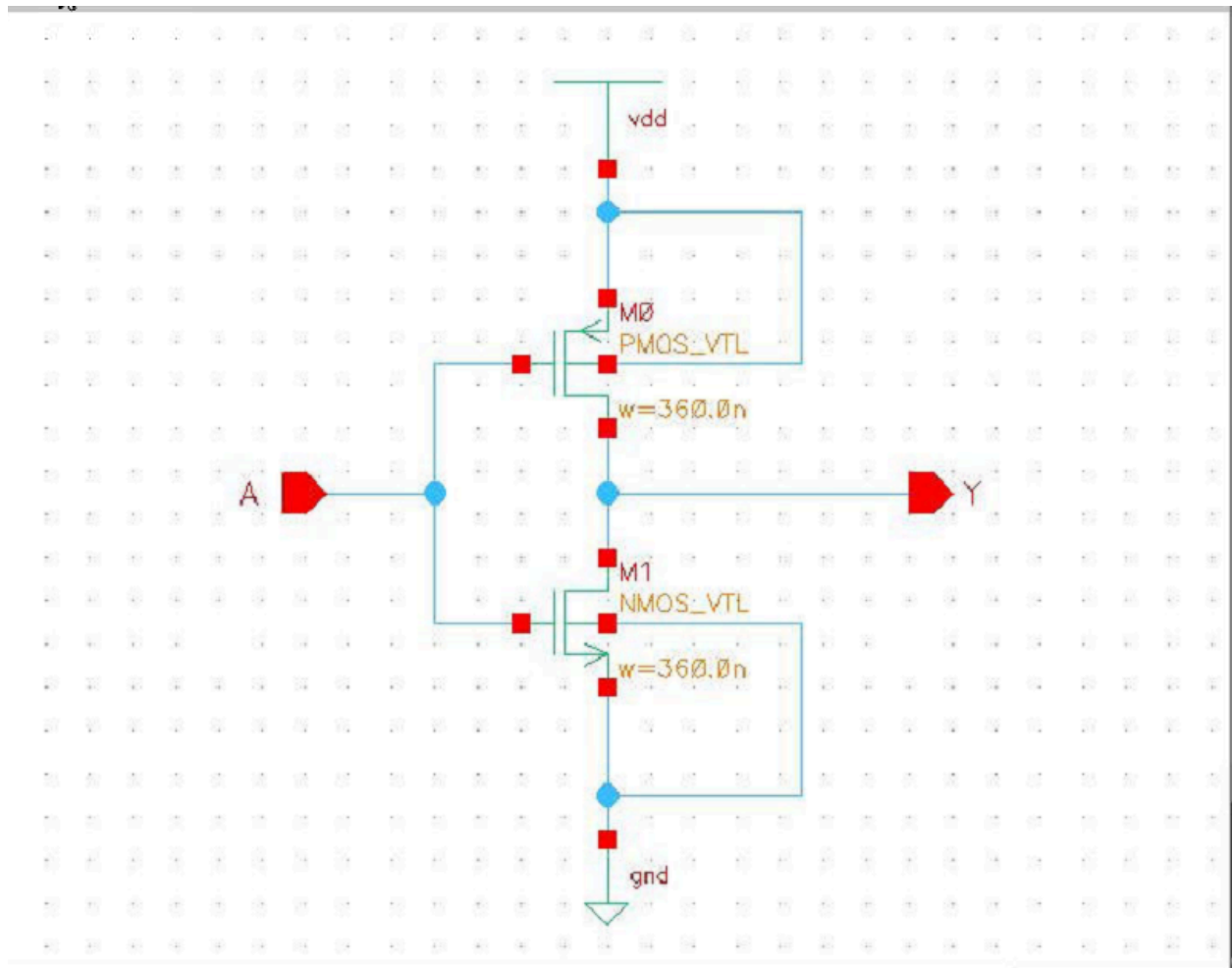

**5) Transistor Dimensions:****Table 8:** Cell and Transistor Dimensions for CMOS Wide Inverter

| Cell Physical Dimensions        |             |            |
|---------------------------------|-------------|------------|
|                                 | X           | Y          |
| Cell Dimension in $\mu\text{m}$ | 50          | 360        |
| Transistor Dimensions           |             |            |
| Transistor Instance Number      | Length (nm) | Width (nm) |
| PMOS_VTL                        | 50          | 360        |
| NMOS_VTL                        | 50          | 360        |

**6) Input X: Output Rise Time Data  $t_r$  (ns):****Table 9:** Transistor Rise Time for CMOS Wide Inverter

| Input X: Output Rise Time Data $t_r$ |                   |   |   |        |   |
|--------------------------------------|-------------------|---|---|--------|---|
| Input rise/fall time (ns)            | Output Load (FOx) |   |   |        |   |
|                                      | 0                 | 1 | 2 | 4      | 8 |
| 0.04                                 | -                 | - | - | 0.0943 | - |

**7) Stack S, Input X: Output Fall Time Data  $t_f$  (ns):****Table 10:** Transistor Fall Time for CMOS Wide Inverter

| Input X: Output Fall Time Data $t_f$ |                   |   |   |        |   |
|--------------------------------------|-------------------|---|---|--------|---|
| Input rise/fall time (ns)            | Output Load (FOx) |   |   |        |   |
|                                      | 0                 | 1 | 2 | 4      | 8 |
| 0.04                                 | -                 | - | - | 0.0301 | - |



### 8) Data Worst Case Low to High Propagation Delay $t_{p_{lh}}$ (ns):

**Table 11:** Data Worst Case Low to High Propagation Delay  $t_{p_{lh}}$  (ns) for CMOS Wide Inverter

| Data Worst Case Low to High Propagation Delay $t_{p_{lh}}$ (ns) |                   |   |   |        |   |
|---|-------------------|---|---|--------|---|
| Input rise/fall time (ns)                                       | Output Load (FOx) |   |   |        |   |
|   | 0                 | 1 | 2 | 4      | 8 |
| 0.04  | -                 | - | - | 0.0292 | - |


### 9) Data Worst Case High to Low Propagation Delay $t_{p_{hl}}$ (ns):

**Table 12:** Data Worst Case High to Low Propagation Delay  $t_{p_{hl}}$  (ns) for CMOS Wide Inverter


| Data Worst Case Low to High Propagation Delay $t_{p_{hl}}$ (ns) |                   |   |   |        |   |
|---|-------------------|---|---|--------|---|
| Input rise/fall time (ns)                                       | Output Load (FOx) |   |   |        |   |
|   | 0                 | 1 | 2 | 4      | 8 |
| 0.04  | -                 | - | - | 0.0733 | - |

### 10) Transient Analysis

**Figure 8:** 50x360 Wide CMOS Transient Analysis Waveform - 1

 


**Figure 9: 50x360 Wide CMOS Transient Analysis Waveform - 2**

  

## 11) DC analysis

**Figure 10: 50x360 Wide CMOS DC Analysis Waveform**



Ken Sutter  
Phil Nevins  
Cody Reid  
Daniel Anishchenko


## ECE-425 Lab 1 Resistive Load Inverter

### 1) Cell Description: Resistive Load Inverter

The Resistive Load Inverter is a type of CMOS inverter that uses a passive resistive load instead of an active load. This acts as a digital logic gate that performs the logical NOT operation. The Resistive Load Inverter has one input and one output. When the input is at a high logic level, the NMOS transistor is on (closed), and the PMOS transistor is off (open). This interrupts the current path through the resistive load, causing the output to be pulled to a low logic level. The Resistive Load inverter is built using one NMOS and one PMOS transistor connected in series through their drains. The input of the Resistive Load inverter is connected to the gates of both transistors. The output of the Resistive Load transistor is connected to the drains of both PMOS and NMOS. The source for the NMOS is connected to ground and the source of PMOS is connected to the power supply (VDD). The Resistive Load inverter offers advantages in terms of power consumption and area efficiency compared to some other load configurations.

### 2) Cell Symbol:

Figure 11: Resistive Inverter Cell symbol

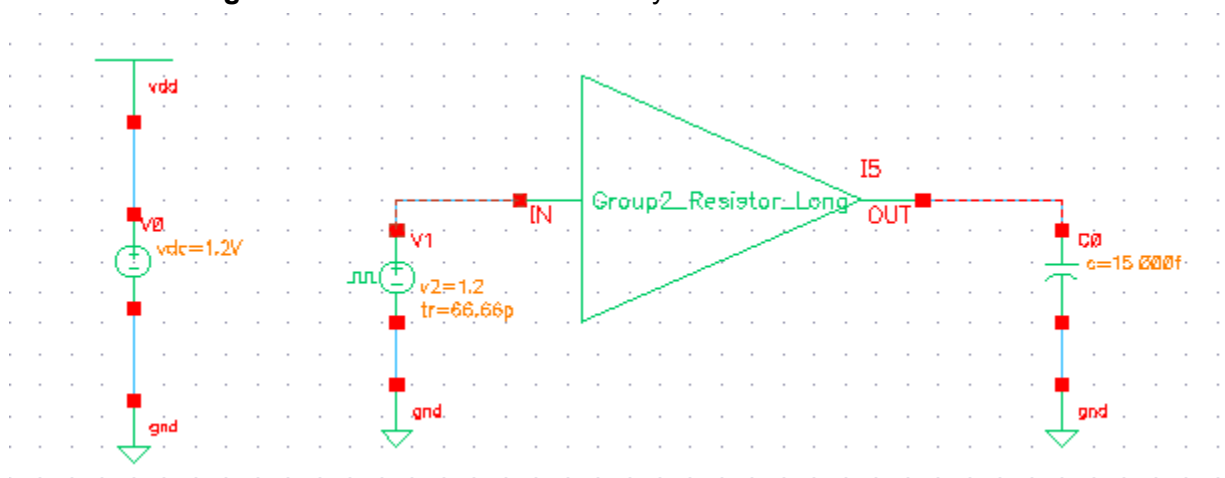


### 3) Cell Truth Table:

**Table 13:** Resistive Load Inverter Truth Table

| Cell Truth Table  |                    |
|-------------------|--------------------|
| Cell Inputs {0,1} | Cell Outputs {H,L} |
| 0                 | H                  |
| 1                 | L                  |

### 4) Cell Schematic Diagram:

**Figure 12:** Resistive Inverter Schematic

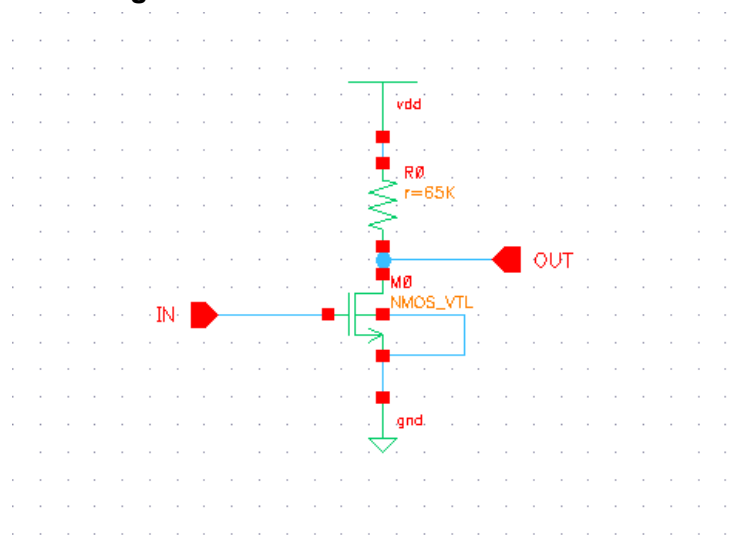

### 5) Transistor Dimensions:

**Table 14:** Cell and Transistor Dimensions for Resistive Load Inverter

| Cell Physical Dimensions        |              |            |
|---------------------------------|--------------|------------|
|                                 | X            | Y          |
| Cell Dimension in $\mu\text{m}$ | 50           | 90         |
| Transistor Dimensions           |              |            |
| Transistor Instance Number      | Length (nm)  | Width (nm) |
| R1                              | 65k $\Omega$ | -          |
| NMOS_VTL                        | 50           | 90         |

**6) Input X: Output Rise Time Data  $t_r$  (ns):****Table 15:** Transistor Rise Time for Resistive Load Inverter

| Input X: Output Rise Time Data $t_r$ |                   |   |   |       |   |
|--------------------------------------|-------------------|---|---|-------|---|
| Input rise/fall time (ns)            | Output Load (FOx) |   |   |       |   |
|                                      | 0                 | 1 | 2 | 4     | 8 |
| 0.04                                 | -                 | - | - | 1.279 | - |

**7) Stack S, Input X: Output Fall Time Data  $t_f$  (ns):****Table 16:** Transistor Fall Time for Resistive Load Inverter

| Input X: Output Fall Time Data $t_f$ |                   |   |   |        |   |
|--------------------------------------|-------------------|---|---|--------|---|
| Input rise/fall time (ns)            | Output Load (FOx) |   |   |        |   |
|                                      | 0                 | 1 | 2 | 4      | 8 |
| 0.04                                 | -                 | - | - | 0.1185 | - |

**8) Data Worst Case Low to High Propagation Delay  $tp_{lh}$  (ns):****Table 17:** Data Worst Case Low to High Propagation Delay  $tp_{lh}$  (ns) for Resistive Load Inverter


| Data Worst Case Low to High Propagation Delay $tp_{lh}$ (ns) |                   |   |   |       |   |
|--|-------------------|---|---|-------|---|
| Input rise/fall time (ns)                                    | Output Load (FOx) |   |   |       |   |
|  | 0                 | 1 | 2 | 4     | 8 |
| 0.04   | -                 | - | - | 0.099 | - |

**9) Data Worst Case High to Low Propagation Delay  $tp_{hl}$  (ns):****Table 18:** Data Worst Case High to Low Propagation Delay  $tp_{hl}$  (ns) for Resistive Load Inverter

| Data Worst Case Low to High Propagation Delay $tp_{hl}$ (ns) |                   |   |   |       |   |
|--|-------------------|---|---|-------|---|
| Input rise/fall time (ns)                                    | Output Load (FOx) |   |   |       |   |
|  | 0                 | 1 | 2 | 4     | 8 |
| 0.04   | -                 | - | - | 0.646 | - |


10) Transient Analysis

Figure 13: Resistive Inverter Transient analysis

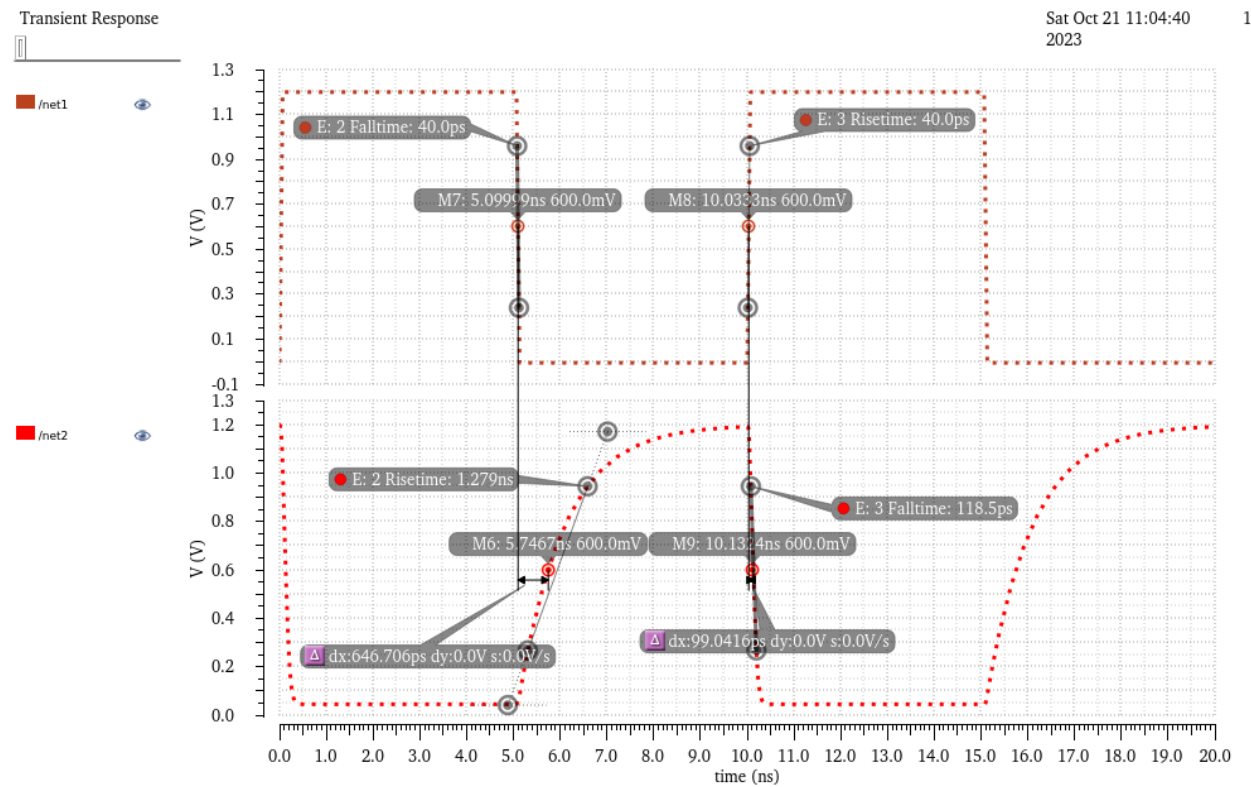

11) DC analysis

Figure 14: Resistive Inverter DC analysis

 


### 1) Cell Description: Long Resistive Load Inverter

The Long Resistive Load Inverter is a type of CMOS inverter that uses a passive resistive load instead of an active load. This acts as a digital logic gate that performs the logical NOT operation. The Long Resistive Load Inverter has one input and one output. When the input A is at a high logic level, the NMOS transistor is on (closed), and the PMOS transistor is off (open). This interrupts the current path through the resistive load, causing the output to be pulled to a low logic level. The Long Resistive Load inverter uses long transistor dimensions. The Long Resistive Load inverter is built using one NMOS and one PMOS transistor connected in series through their drains. The input of the Long Resistive Load inverter is connected to the gates of both transistors. The output of the Long Resistive Load transistor is connected to the drains of both PMOS and NMOS. The source for the NMOS is connected to ground and the source of PMOS is connected to the power supply (VDD). The Long Resistive Load inverter offers advantages in terms of power consumption and area efficiency compared to some other load configurations.

### 2) Cell Symbol:

Figure 15: Long resistive Inverter Cell symbol

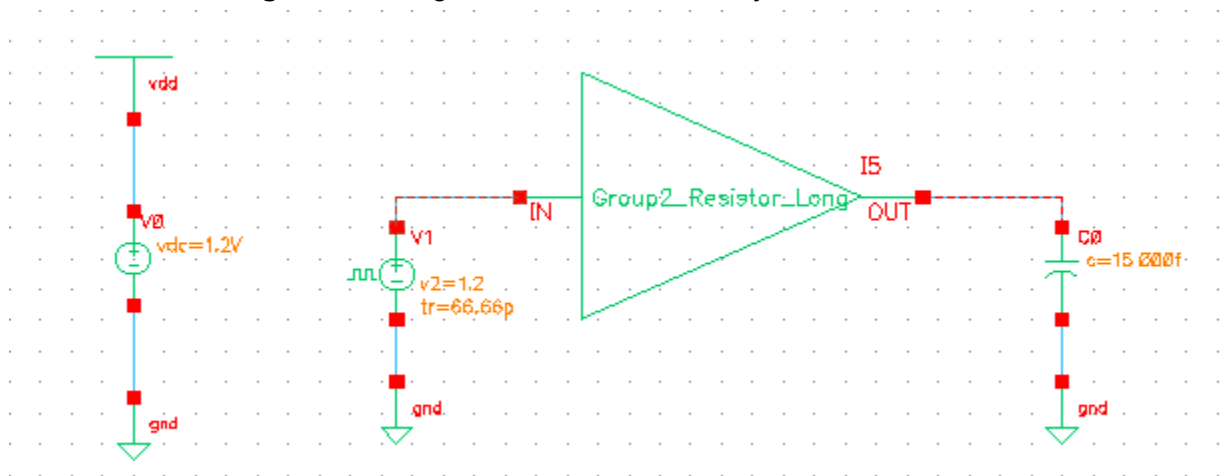


### 3) Cell Truth Table:

Table 19: Long Resistive Load Inverter Truth Table

| Cell Truth Table  |                    |
|-------------------|--------------------|
| Cell Inputs {0,1} | Cell Outputs {H,L} |
| 0                 | H                  |
| 1                 | L                  |

#### 4) Cell Schematic Diagram:

**Figure 16:** Long resistive Inverter schematic

 

#### 5) Transistor Dimensions:

**Table 20:** Cell and Transistor Dimensions for Long Resistive Load Inverter

| Cell Physical Dimensions        |               |            |
|---------------------------------|---------------|------------|
|                                 | X             | Y          |
| Cell Dimension in $\mu\text{m}$ | 50            | 90         |
| Transistor Dimensions           |               |            |
| Transistor Instance Number      | Length (nm)   | Width (nm) |
| R1                              | 155k $\Omega$ | -          |
| NMOS_VTL                        | 50            | 90         |

#### 6) Input X: Output Rise Time Data $t_r$ (ns):

**Table 21:** Transistor Rise Time for Long Resistive Load Inverter

| Input X: Output Rise Time Data $t_r$ |                   |   |   |       |   |
|--------------------------------------|-------------------|---|---|-------|---|
| Input rise/fall time (ns)            | Output Load (FOx) |   |   |       |   |
|                                      | 0                 | 1 | 2 | 4     | 8 |
| 0.04                                 | -                 | - | - | 1.964 | - |



**7) Stack S, Input X: Output Fall Time Data  $t_f$  (ns):**

**Table 22:** Transistor Fall Time for Long Resistive Load Inverter

| Input X: Output Fall Time Data $t_f$ |                   |   |   |       |   |
|--------------------------------------|-------------------|---|---|-------|---|
| Input rise/fall time (ns)            | Output Load (FOx) |   |   |       |   |
|                                      | 0                 | 1 | 2 | 4     | 8 |
| 0.04                                 | -                 | - | - | 0.104 | - |

**8) Data Worst Case Low to High Propagation Delay  $tp_{lh}$  (ns):**

**Table 23:** Data Worst Case Low to High Propagation Delay  $tp_{lh}$  (ns) for Long Resistive Load Inverter

| Data Worst Case Low to High Propagation Delay $tp_{lh}$ (ns) |                   |   |   |       |   |
|--|-------------------|---|---|-------|---|
| Input rise/fall time (ns)                                    | Output Load (FOx) |   |   |       |   |
|  | 0                 | 1 | 2 | 4     | 8 |
| 0.04   | -                 | - | - | 0.077 | - |


**9) Data Worst Case High to Low Propagation Delay  $tp_{hl}$  (ns):**

**Table 24:** Data Worst Case High to Low Propagation Delay  $tp_{hl}$  (ns) for Long Resistive Load Inverter

| Data Worst Case Low to High Propagation Delay $tp_{hl}$ (ns) |                   |   |   |       |   |
|--|-------------------|---|---|-------|---|
| Input rise/fall time (ns)                                    | Output Load (FOx) |   |   |       |   |
|  | 0                 | 1 | 2 | 4     | 8 |
| 0.04   | -                 | - | - | 1.593 | - |


10) Transient Analysis

Figure 17: Long resistive Inverter Transient Analysis

 

11) DC analysis

Figure 18: Long resistive Inverter DC analysis

 

Ken Sutter  
Phil Nevins  
Cody Reid  
Daniel Anishchenko


## ECE-425 Lab 1 Enhancement Mode NFET Inverter

### 1) Cell Description: Enhancement Mode NFET Inverter (Short)

The Enhancement Mode NFET (N-Channel Field-Effect Transistor) inverter is a digital logic gate that uses a single N-channel MOSFET for inverting the input signal. The Enhancement Mode NFET inverter is a digital logic gate that performs the logical NOT operation. It has one input and one output. When input is high, output is low, and when input is low, output is high. When the input is at a high logic level, the NFET is on (closed). This allows current to flow from the drain to the source, connecting the output Y to ground (GND) and pulling it to a low logic level. The Enhancement Mode NFET is built with source connected to ground, drain connected to the output and the gate connected to the input. The Enhancement Mode NFET inverter is relatively simple and is often used in low-power applications or as part of more complex digital circuits. It is commonly found in integrated circuits where N-channel MOSFETs are used for their simplicity and efficient operation when driving a low impedance output.

### 2) Cell Symbol:

**Figure 19:** 350x90 Enhancement NFET Inverter TB Schematic

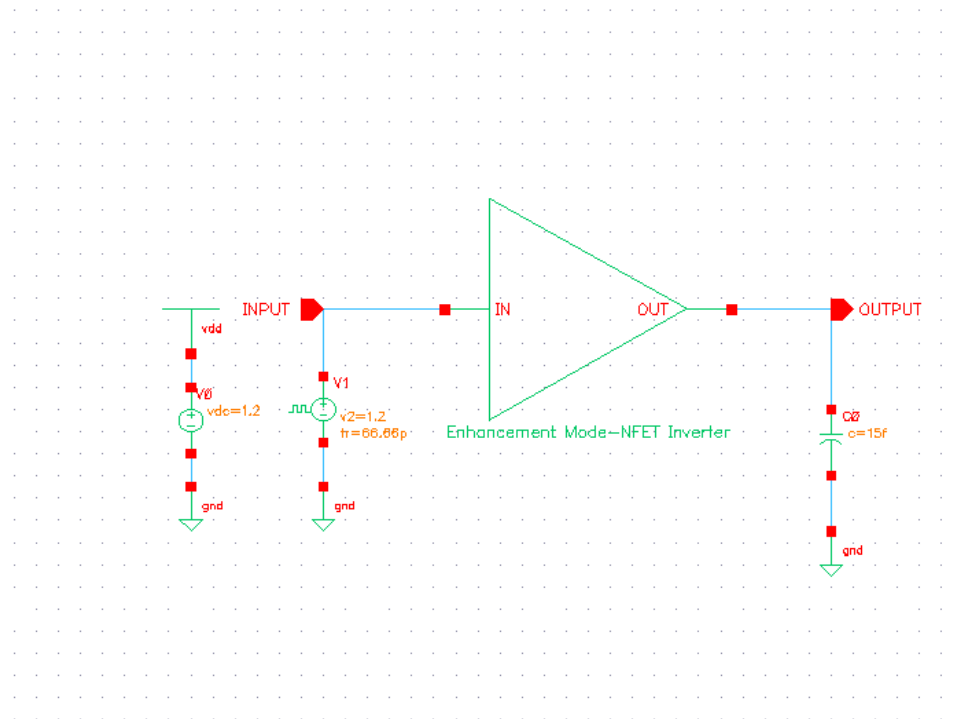


### 3) Cell Truth Table:

**Table 25:** Enhancement mode NFET Inverter Truth Table

| Cell Truth Table  |                    |
|-------------------|--------------------|
| Cell Inputs {0,1} | Cell Outputs {H,L} |
| 0                 | H                  |
| 1                 | L                  |

### 4) Cell Schematic Diagram:

**Figure 20:** 350x90 Enhancement NFET Inverter TB Schematic

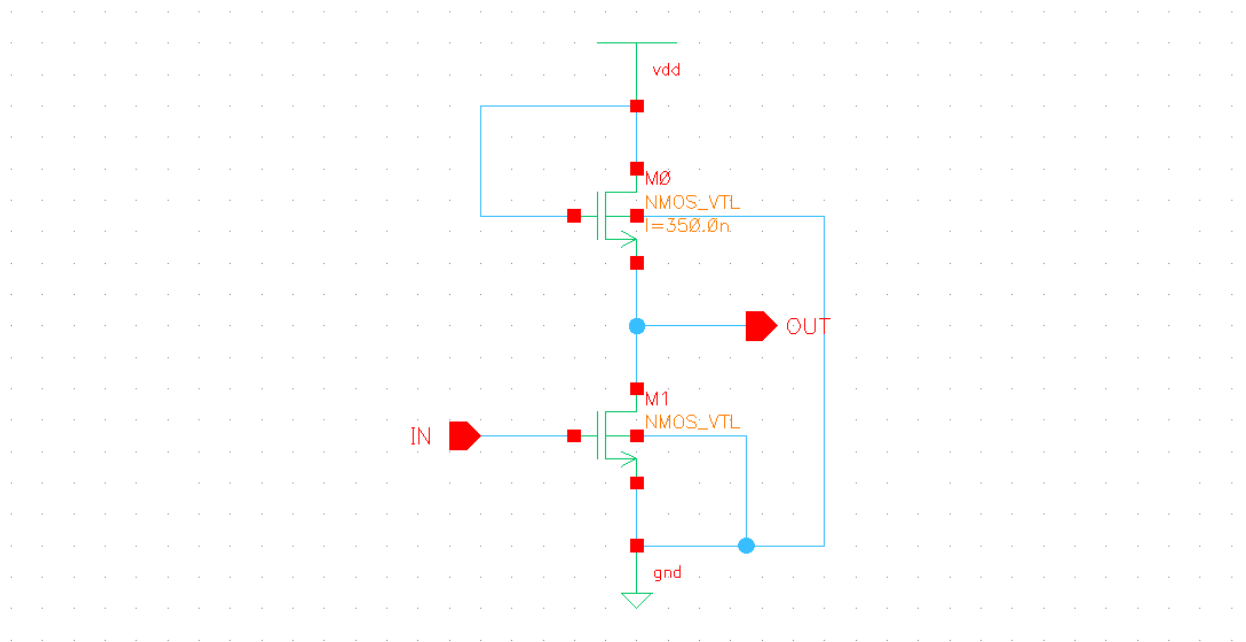

### 5) Transistor Dimensions:

**Table 26:** Cell and Transistor Dimensions Enhancement Mode NFET Inverter

| Cell Physical Dimensions        |             |            |
|---------------------------------|-------------|------------|
|                                 | X           | Y          |
| Cell Dimension in $\mu\text{m}$ | 50          | 90         |
| Transistor Dimensions           |             |            |
| Transistor Instance Number      | Length (nm) | Width (nm) |
| NMOS_VTL (pull up)              | 50          | 90         |
| NMOS_VTL (pull down)            | 350         | 90         |

**6) Input X: Output Rise Time Data  $t_r$  (ns):****Table 27:** Transistor Rise Time for Enhancement Mode NFET Inverter

| Input X: Output Rise Time Data $t_r$ |                   |   |   |       |   |
|--------------------------------------|-------------------|---|---|-------|---|
| Input rise/fall time (ns)            | Output Load (FOx) |   |   |       |   |
|                                      | 0                 | 1 | 2 | 4     | 8 |
| 0.04                                 | -                 | - | - | 1.241 | - |

**7) Stack S, Input X: Output Fall Time Data  $t_f$  (ns):****Table 28:** Transistor Fall Time for Enhancement Mode NFET Inverter

| Input X: Output Fall Time Data $t_f$ |                   |   |   |         |   |
|--------------------------------------|-------------------|---|---|---------|---|
| Input rise/fall time (ns)            | Output Load (FOx) |   |   |         |   |
|                                      | 0                 | 1 | 2 | 4       | 8 |
| 0.04                                 | -                 | - | - | 0.07648 | - |

**8) Data Worst Case Low to High Propagation Delay  $tp_{lh}$  (ns):****Table 29:** Data Worst Case Low to High Propagation Delay  $tp_{lh}$  (ns) for Enhancement Mode NFET Inverter

| Data Worst Case Low to High Propagation Delay $tp_{lh}$ (ns) |                   |   |   |        |   |
|--|-------------------|---|---|--------|---|
| Input rise/fall time (ns)                                    | Output Load (FOx) |   |   |        |   |
|  | 0                 | 1 | 2 | 4      | 8 |
| 0.04   | -                 | - | - | 0.3516 | - |

**9) Data Worst Case High to Low Propagation Delay  $tp_{hl}$  (ns):****Table 30:** Data Worst Case High to Low Propagation Delay  $tp_{hl}$  (ns) for Enhancement Mode NFET Inverter

| Data Worst Case High to Low Propagation Delay $tp_{hl}$ (ns) |                   |   |   |         |   |
|--|-------------------|---|---|---------|---|
| Input rise/fall time (ns)                                    | Output Load (FOx) |   |   |         |   |
|  | 0                 | 1 | 2 | 4       | 8 |
| 0.04   | -                 | - | - | 0.06284 | - |

## 10) Transient Analysis

Figure 21: 350x90 Enhancement NFET Inverter Transient - 1



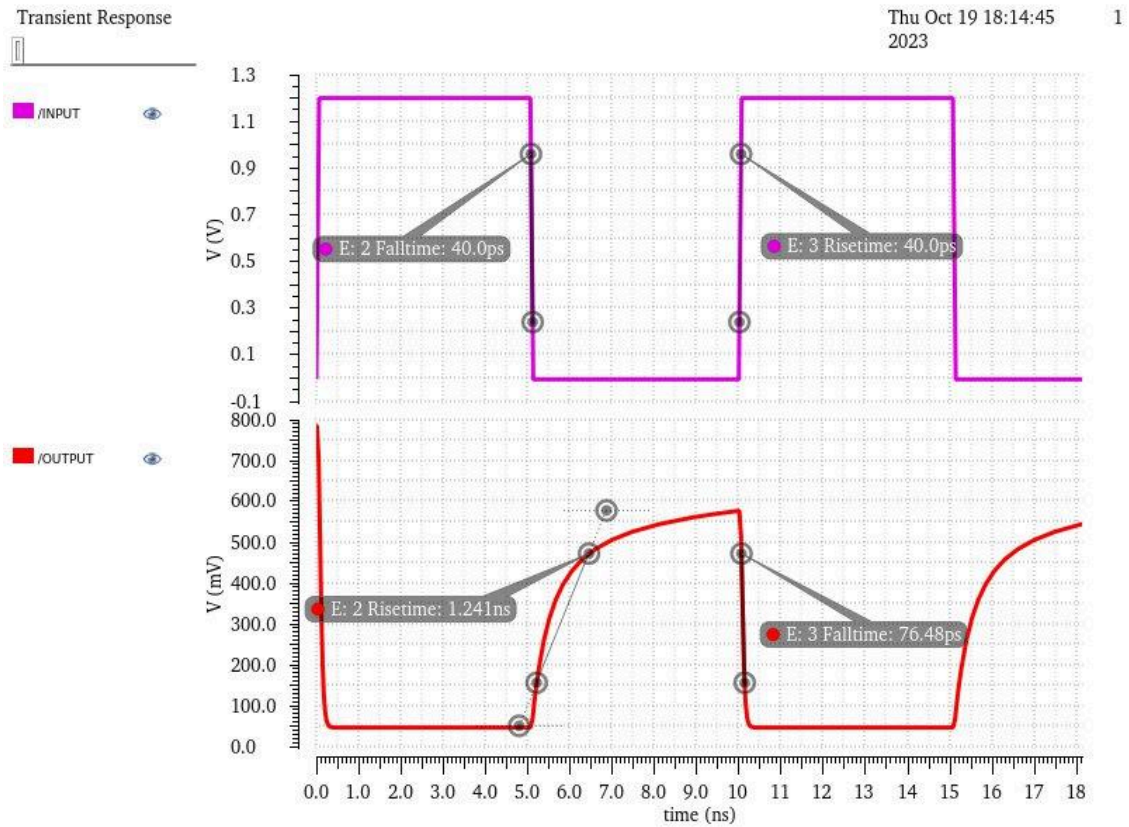


Figure 22: 350x90 Enhancement NFET Inverter Transient - 2

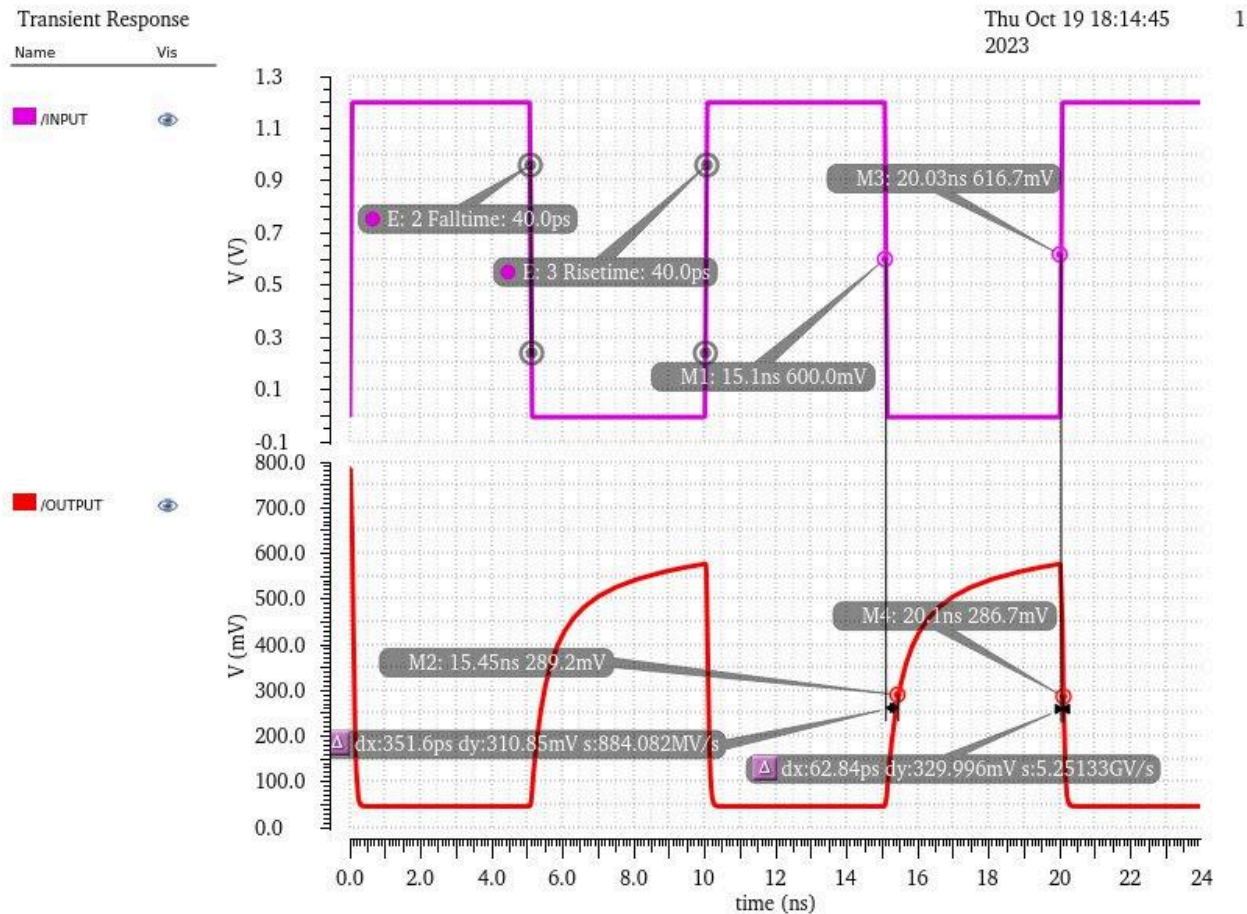

## 11) DC analysis

Figure 23: 350x90 Enhancement NFET Inverter DC Analysis

 




## 1) Cell Description: Long Enhancement Mode NFET Inverter (Long)

The Long Enhancement Mode NFET (N-Channel Field-Effect Transistor) inverter is a digital logic gate that uses a single N-channel MOSFET for inverting the input signal. The Long Enhancement Mode NFET inverter is a digital logic gate that performs the logical NOT operation. It has one input and one output. When the input is at a high logic level, the NFET is on (closed). This allows current to flow from the drain to the source, connecting the output Y to ground (GND) and pulling it to a low logic level. The Long Enhancement Mode NFET inverter uses long transistor dimensions. The Long Enhancement Mode NFET is built with source connected to ground, drain connected to the output and the gate connected to the input. The Long Enhancement Mode NFET inverter is relatively simple and is often used in low-power applications or as part of more complex digital circuits. It is commonly found in integrated circuits where N-channel MOSFETs are used for their simplicity and efficient operation when driving a low impedance output.

## 2) Cell Symbol:

**Figure 24:** 1000x90 Enhancement NFET Inverter TB Schematic

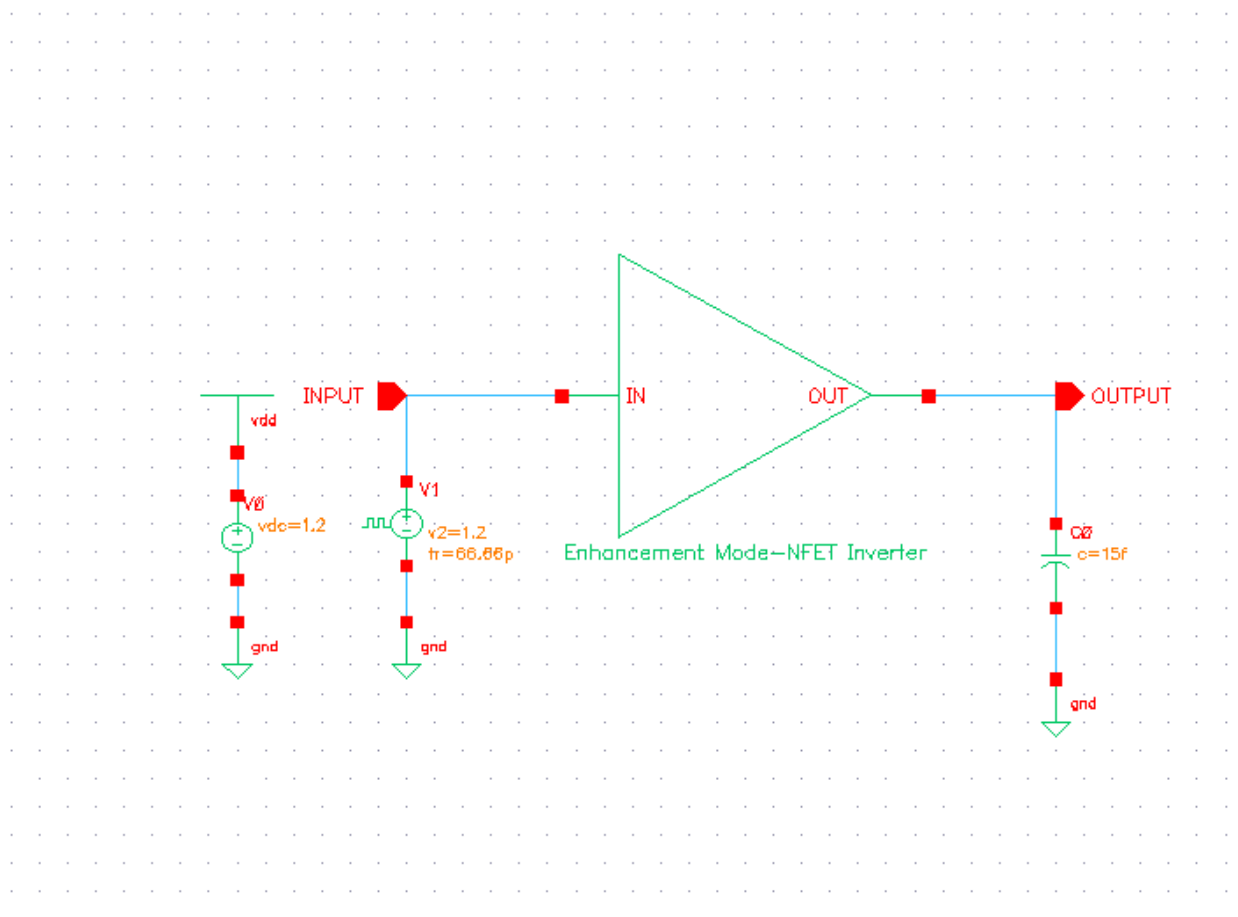


3) Cell Truth Table:

Table 31: Long Enhancement mode NFET Inverter Truth Table

| Cell Truth Table  |                    |
|-------------------|--------------------|
| Cell Inputs {0,1} | Cell Outputs {H,L} |
| 0                 | H                  |
| 1                 | L                  |

4) Cell Schematic Diagram:

Figure 25: 1000x90 Enhancement NFET Inverter TB Schematic

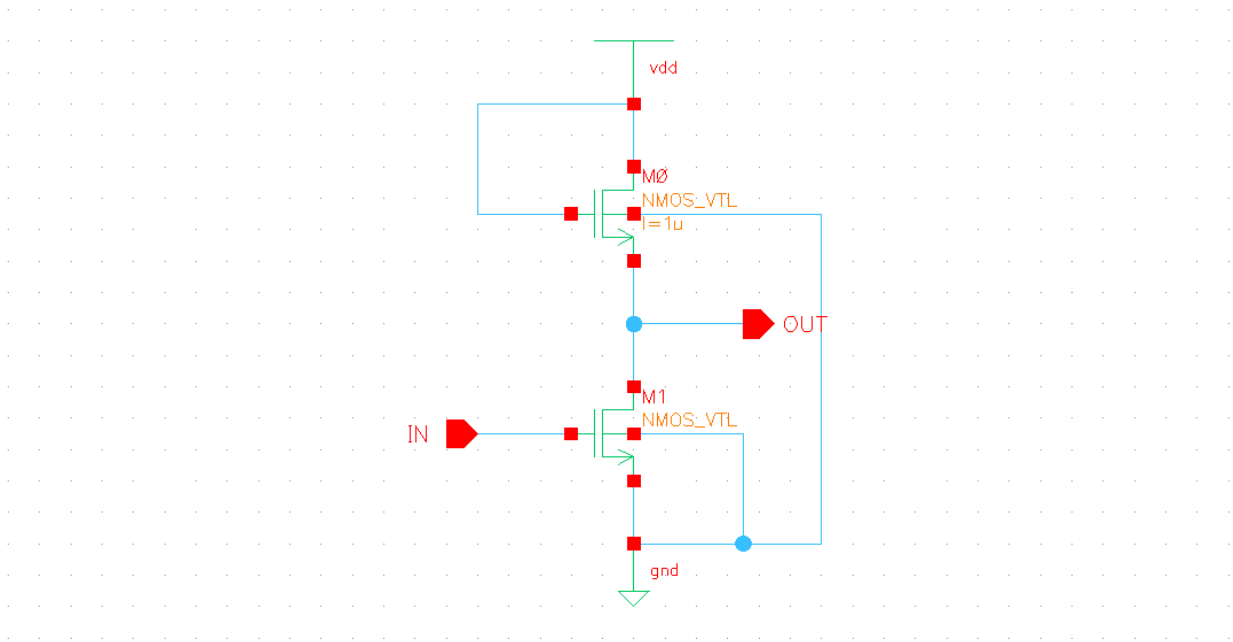

5) Transistor Dimensions:

Table 32: Cell and Transistor Dimensions for Long Enhancement Mode NFET Inverter

| Cell Physical Dimensions        |             |            |
|---------------------------------|-------------|------------|
|                                 | X           | Y          |
| Cell Dimension in $\mu\text{m}$ | 50          | 90         |
| Transistor Dimensions           |             |            |
| Transistor Instance Number      | Length (nm) | Width (nm) |
| NMOS_VTL (Pull Down)            | 50          | 90         |
| NMOS_VTL (Pull Up)              | 1000        | 90         |

**6) Input X: Output Rise Time Data  $t_r$  (ns):****Table 33:** Transistor Rise Time for Long Enhancement Mode NFET Inverter

| Input X: Output Rise Time Data $t_r$ |                   |   |   |       |   |
|--------------------------------------|-------------------|---|---|-------|---|
| Input rise/fall time (ns)            | Output Load (FOx) |   |   |       |   |
|                                      | 0                 | 1 | 2 | 4     | 8 |
| 0.04                                 | -                 | - | - | 1.998 | - |

**7) Stack S, Input X: Output Fall Time Data  $t_f$  (ns):****Table 34:** Transistor Fall Time for Long Enhancement Mode NFET Inverter

| Input X: Output Fall Time Data $t_f$ |                   |   |   |         |   |
|--------------------------------------|-------------------|---|---|---------|---|
| Input rise/fall time (ns)            | Output Load (FOx) |   |   |         |   |
|                                      | 0                 | 1 | 2 | 4       | 8 |
| 0.04                                 | -                 | - | - | 0.08068 | - |

**8) Data Worst Case Low to High Propagation Delay  $tp_{lh}$  (ns):****Table 35:** Data Worst Case Low to High Propagation Delay  $tp_{lh}$  (ns) for Long Enhancement Mode NFET Inverter


| Data Worst Case Low to High Propagation Delay $tp_{lh}$ (ns) |                   |   |   |        |   |
|--|-------------------|---|---|--------|---|
| Input rise/fall time (ns)                                    | Output Load (FOx) |   |   |        |   |
|  | 0                 | 1 | 2 | 4      | 8 |
| 0.04   | -                 | - | - | 0.8283 | - |

**9) Data Worst Case High to Low Propagation Delay  $tp_{hl}$  (ns):****Table 36:** Data Worst Case High to Low Propagation Delay  $tp_{hl}$  (ns) for Long Enhancement Mode NFET Inverter

| Data Worst Case High to Low Propagation Delay $tp_{hl}$ (ns) |                   |   |   |         |   |
|--|-------------------|---|---|---------|---|
| Input rise/fall time (ns)                                    | Output Load (FOx) |   |   |         |   |
|  | 0                 | 1 | 2 | 4       | 8 |
| 0.04   | -                 | - | - | 0.05982 | - |

## 10) Transient Analysis

Figure 26: 1000x90 Enhancement NFET Inverter Transient - 1

 


**Figure 27: 1000x90 Enhancement NFET Inverter Transient - 2**

 Transient Response


Thu Oct 19 18:57:33  
2023

1



11) DC analysis

Figure 28: 1000x90 Enhancement NFET Inverter DC

 

Ken Sutter  
Phil Nevins  
Cody Reid  
Daniel Anishchenko

## ECE-425 Lab 1 Questions and Comparison

### Inverter comparison by performance

Prepare two additional tables (shown below) comparing the performance of the six inverters.

**Table 37:** Transient Analysis Comparison (ns)

| Type                        | $t_{p_{lh}}$ | $t_{p_{hl}}$ | $t_r$  | $t_f$   |
|-----------------------------|--------------|--------------|--------|---------|
| CMOS                        | 0.0736       | 0.0937       | 0.3949 | 0.1155  |
| CMOS_Wide                   | 0.0292       | 0.0270       | 0.0943 | 0.0301  |
| Enhancement mode NFET_Short | 0.3516       | 0.06284      | 1.241  | 0.07648 |
| Enhancement mode NFET_Long  | 0.8283       | 0.05982      | 1.998  | 0.08068 |
| Resistive Load              | 1.593        | 0.6467       | 1.279  | 0.1185  |
| Resistive Load_Long         | 0.077        | 1.593        | 1.964  | 0.104   |

**Table 38:** DC Analysis Comparison (mV)

| Type                        | $V_{IH\_DC}$ | $V_{IL\_DC}$ | $V_{OH\_DC}$ | $V_{OL\_DC}$ |
|-----------------------------|--------------|--------------|--------------|--------------|
| CMOS                        | 613.3        | 369.374      | 369.374      | 613.3        |
| CMOS_Wide                   | 614.032      | 369.597      | 369.597      | 614.032      |
| Enhancement mode NFET_Short | 624.679      | 344.751      | 508.485      | 117.377      |
| Enhancement mode NFET_Long  | 550.588      | 270.727      | 528.809      | 66.047       |
| Resistive Load              | 667.373      | 301.999      | 301.999      | 667.373      |
| Resistive Load_Long         | 576.624      | 252.654      | 252.654      | 576.624      |

### Part 5: Questions for Lab 1

**Answer the following questions and include them in your report.**

**1. Explain in your own words the variation of the DC output voltages  $V_{OH}$  and  $V_{OL}$  for the four inverters? In particular focus on the differences noted earlier in the NFET connected inverters and explain in your own words the variation of the switching times for all the inverters?**

**CMOS Inverter:**

The  $V_{OH}$  of a standard CMOS inverter is relatively close to the supply voltage; this makes it ideal for logic high levels. The  $V_{OL}$  is close to the ground voltage, which is suitable for logic low levels. CMOS inverters generally offer fast switching times due to their complementary structure.

**CMOS Wide Inverter:**

This is a variation of the CMOS inverter with wider transistors, which can help reduce resistive losses and improve performance.  $V_{OH}$  and  $V_{OL}$  typically remain close to  $V_{DD}$  and GND, similar to the standard CMOS inverter. The wider transistors can lead to slightly faster switching times and better performance.

**NFET Resistive Load Inverter:**

The  $V_{OH}$  of an NFET resistive load inverter may be lower than the supply voltage  $V_{DD}$  due to the voltage drop across the load resistor. The  $V_{OL}$  is close to GND. These inverters tend to have slower switching times compared to CMOS inverters because the load resistor introduces additional capacitance.

**Long NFET Resistive Load Inverter:**

Similar to the NFET resistive load inverter but with longer NFET transistors.  $V_{OH}$  and  $V_{OL}$  are affected similarly to the standard NFET resistive load inverter. Longer NFET transistors can further increase the switching times due to their increased capacitance.

**NFET Enhancement Mode Inverter:**

The  $V_{OH}$  of an NFET enhancement mode inverter is typically lower than  $V_{DD}$  due to the voltage drop across the NFET transistor when it's on. The  $V_{OL}$  is close to GND. These inverters tend to have slower switching times compared to CMOS inverters because of the characteristics of enhancement-mode transistors.

**Long NFET Enhancement Mode Inverter:**

Same as the NFET enhancement mode inverter but with longer NFET transistors.  $V_{OH}$  and  $V_{OL}$  are affected similarly to the standard NFET enhancement mode inverter. Longer NFET



transistors can further increase the switching times due to their increased capacitance and the nature of enhancement-mode transistors.

The key differences in  $V_{OH}$  and  $V_{OL}$  among these inverters are from their transistor configurations and load types. The switching times are affected by transistor characteristics, gate capacitance, and resistive or capacitive loads. CMOS-based inverters tend to offer faster switching times and more defined high and low voltage levels compared to NFET-based inverters.

**2. List out the major drawbacks and benefits of using a NFET load and resistor for signal inversion from area, VTC (Voltage Transfer Characteristic), noise margin, leakage and fabrication point of view. Why do you think CMOS has become so popular in recent times?**

Using an NFET load and a resistor for signal inversion in digital circuits, as opposed to CMOS logic, has both advantages and disadvantages in terms of area, VTC, noise margin, leakage, and fabrication.

**The NFET load and resistor for signal inversion:**

NFET load and resistor configurations can be smaller in size compared to CMOS inverters. This is helpful when you have an area constraint issue. The circuit design using an NFET load and resistor is simpler, it uses fewer components and can create a more simplified design. NFET inverters can provide better performance in analog applications, as they have a more linear voltage transfer characteristic (VTC) compared to CMOS

**Disadvantages of NFET load and resistor for signal inversion:**

NFET load inverters typically have lower noise margins compared to CMOS, making them more susceptible to noise interference and signal degradation. NFET transistors can have higher leakage current compared to their CMOS counterparts, leading to higher static power consumption. NFET load inverters may have slower switching speeds due to the higher resistance of the load resistor, which can be a downside in high-speed digital applications. NFET inverters are not ideal for digital logic because of their reduced noise margins and slower switching speeds. CMOS is much more efficient for this application.

**Why CMOS has become popular in recent times:**

CMOS technology has gained popularity and become the main choice for digital integrated circuits. CMOS logic is known for its power efficiency. It consumes little power when not switching. CMOS logic provides high noise margins, making it work well against noise and is great for high-performance digital applications. CMOS can achieve high-speed operation, making it useful for a wide range of digital applications. CMOS technology can be scaled down to smaller feature sizes, allowing for the integration of a large number of transistors on a single chip, which is essential for modern semiconductor technology.

**3. What happens if PMOS and NMOS are interchanged in an inverter connection? Where should you measure the output to get the desired inverted signal after interchanging their positions?**

If you interchange the PMOS and NMOS transistors in an inverter connection, it reverses the behavior of the circuit. Instead of producing a logical NOT output, it will produce a logical NOT of the original input signal. In other words, it will act as a buffer, or non-inverting gate. To measure the output of the circuit to get the inverted signal after switching the positions of the PMOS and NMOS transistors, you should measure the voltage at the output node of the circuit. This is the same place the output signal is taken in a normal inverter. The voltage at the output node will be the logical NOT of the input signal, and it will provide the desired inverted output.

**4. What are the roles and responsibilities of each member of your lab team? Who did what part of the lab?**

Cody Reid: Configured and analyzed both CMOS 50x90 and CMOS 50x360 circuits. Assisted with lab write up, figures, and formatting.

Daniel Anishchenko: Built and simulated the resistive circuits as well worked on the formal report.

Ken Sutter: Working on formal report, answering lab questions, doing circuit calculations, documenting team work, helping design circuits.

Phil Nevins: Built and simulated enhancement mode NFET as well as formal report